

1. (69 points)

Team Number

KEY

ZIPGRADE.COM

26 Circuits (9110)

- | | | | | | |
|----|---|-----|--|----|--|
| 1 | <input type="radio"/> A <input checked="" type="radio"/> B <input checked="" type="radio"/> C <input type="radio"/> D | 13 | <input type="radio"/> A <input checked="" type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E | 29 | <input type="radio"/> A <input type="radio"/> B <input checked="" type="radio"/> C <input type="radio"/> D <input type="radio"/> E |
| 2 | <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input checked="" type="radio"/> D <input type="radio"/> E | 14 | <input type="radio"/> A <input type="radio"/> B <input checked="" type="radio"/> C <input type="radio"/> D | 30 | <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input checked="" type="radio"/> E |
| 3 | <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input checked="" type="radio"/> E | 15 | <input checked="" type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E | 31 | <input type="radio"/> A <input type="radio"/> B <input checked="" type="radio"/> C <input type="radio"/> D <input type="radio"/> E |
| 4 | <input checked="" type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E | 16 | <input type="radio"/> A <input checked="" type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E | 32 | <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input checked="" type="radio"/> D <input type="radio"/> E |
| 5a | <input type="radio"/> A <input type="radio"/> B <input checked="" type="radio"/> C <input type="radio"/> D <input type="radio"/> E | 17 | <input checked="" type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input checked="" type="radio"/> D <input checked="" type="radio"/> E | 33 | <input type="radio"/> A <input type="radio"/> B <input checked="" type="radio"/> C <input type="radio"/> D <input type="radio"/> E |
| 5b | <input checked="" type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D | 18 | <input checked="" type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E | 34 | <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input checked="" type="radio"/> E |
| 6a | <input type="radio"/> A <input checked="" type="radio"/> B <input type="radio"/> C <input type="radio"/> D | 19 | <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input checked="" type="radio"/> E | 35 | <input type="radio"/> A <input checked="" type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E |
| 6b | <input type="radio"/> A <input checked="" type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E | 20 | <input checked="" type="radio"/> A <input type="radio"/> B <input checked="" type="radio"/> C <input type="radio"/> D | 36 | <input type="radio"/> A <input checked="" type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E |
| 6c | <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input checked="" type="radio"/> D | 21a | <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input checked="" type="radio"/> D <input type="radio"/> E | | |
| 6d | <input checked="" type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D | 21b | <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input checked="" type="radio"/> E | | |
| 7a | <input checked="" type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E | 21c | <input checked="" type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D | | |
| 7b | <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input checked="" type="radio"/> D | 22 | <input type="radio"/> A <input checked="" type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E | | |
| 7c | <input checked="" type="radio"/> A <input type="radio"/> B <input checked="" type="radio"/> C <input type="radio"/> D <input type="radio"/> E | 23 | <input type="radio"/> A <input checked="" type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E | | |
| 8 | <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input checked="" type="radio"/> E | 24 | <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input checked="" type="radio"/> E | | |
| 9 | <input checked="" type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E | 25 | <input type="radio"/> A <input checked="" type="radio"/> B <input type="radio"/> C <input type="radio"/> D | | |
| 10 | <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input checked="" type="radio"/> E | 26 | <input type="radio"/> A <input checked="" type="radio"/> B <input type="radio"/> C <input type="radio"/> D | | |
| 11 | <input type="radio"/> A <input type="radio"/> B <input checked="" type="radio"/> C <input type="radio"/> D <input type="radio"/> E | 27 | <input type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input checked="" type="radio"/> D | | |
| 12 | <input type="radio"/> A <input type="radio"/> B <input checked="" type="radio"/> C <input type="radio"/> D <input type="radio"/> E | 28 | <input checked="" type="radio"/> A <input type="radio"/> B <input type="radio"/> C <input type="radio"/> D <input type="radio"/> E | | |

Free Response Questions

37. (a) (1 point) _____ **Series** _____
(b) (1 point) _____ **6Ω** _____
(c) (1 point) _____ **500 mA** _____
(d) (1 point) _____ **500 mA** _____
(e) (3 points)

Solution: No (1) because the voltage drop across the resistor is >1 V (2)

- (f) (2 points)

Solution: The $1\text{ M}\Omega$ (1) because it's the largest, minimizing the change in resistance, and thus is closest to the infinite resistance that is equivalent to not having a parallel resistor (1 for anything about how an open circuit is infinite resistance, this minimizes the change in resistance; 0.5 for just saying it's the biggest).

- (g) i. (2 points) _____ **1.33 A (1 for value)** _____
ii. (2 points) _____ **1.33 A (1 for value)** _____
iii. (4 points)

Solution: $I_L = I_C = I_R = 0.25\text{ A}$ (1 point for all 3 values being equal, 1 point for each correct value)

- iv. (2 points) _____ **m/n (all or nothing)** _____

38. (a) (1 point) _____ **1000** _____
(b) (2 points)

Solution: Kirchhoff's current law/junction rule/first law

(c) (2 points) _____ **7 A**

(d) (2 points) _____ **9 A**

39. (a) (2 points)

Solution: $I_1 = I_2 = 0.2A$ (1 for both being equal, 1 for either being the correct value)

(b) (2 points) _____ **2Ω (2)**

(c) (3 points)

Solution: 20Ω (3 points if correct, 1 point for attempt)

(d) (1 point) _____ **$3/5$ or **.6 A****

(e) (1 point) _____ **$3/10$ or **.3 A****

(f) (1 point) _____ **$3/10$ or **.3 A****

(g) (1 point) _____ **$1/10$ or **.1 A****

(h) (1 point) _____ **$1/15$ or **0.067 A****

(i) (2 points)

Solution: $108/25$ or **4.32 Watts (1 for unit, 2 for answer)**

40. (TB #3)

(a) (1 point) _____ **Tesla(s)**

(b) (2 points) _____ **10^4 (no partial credit)**

(c) (1 point) _____ **Same direction**

(d) (2 points) _____ **D**

(e) (3 points)

Solution: 0.333 G, out of the page (2 for value, 1 for direction). 1 partial credit if they write 1 G

(f) (3 points)

Solution: 3.33 G, into the page (2 for value, 1 for direction). 1 partial credit if they write 2 G or 1.33 G

(g) (3 points)

Solution: 3 G, into the page (2 for value, 1 for direction). 1 partial credit if they write 1 G or 2 G

(h) (3 points)

Solution: 3.6 G, out of the page (2 for value, 1 for direction). 1 partial credit if they write 4 G

(i) (3 points)

Solution: $3.51 \cdot 10^{-21}$ to the left N, out of the page (2 for value, 1 for direction).

(j) (3 points)

Solution: 0 force applied (all or nothing because there is no force and thus no direction)

41. (a) (3 points)

Solution: $\frac{3-V_1}{6} = \frac{V_1-V_2}{6} + \frac{V_1-V_3}{8}$ (1 point per term. If a term is on the opposite side, give 0.5 points instead)

- (b) (2 points) _____ **12/7 or 1.714 V**
- (c) (2 points) _____ **15/14 or 1.071 V**
- (d) (2 points) _____ **6/7 or 0.857 V**
- (e) (2 points)

Solution: 3/14 or 0.214 A (1 point for positive sign, 1 points for value). ONLY 1 point for 1/6 or 0.167 A

(f) (2 points)

Solution: 3/28 or 0.107 A (1 point for positive sign, 1 points for value). ONLY 1 point for 1/4 or 0.25 A

(g) (2 points)

Solution: $3/14$ or 0.214 A (1 point for positive sign, 1 points for value). ONLY 1 point for $1/8$ or 0.125 A

42. (TB #1)

(a) (1 point) _____ **The 24Ω resistor in the top right**

(b) (1 point)

Solution: $\frac{1944}{505}$ or 3.850 V

(c) (1 point)

Solution: $\frac{1827}{505}$ or 3.618 V

(d) (1 point)

Solution: $-\frac{1176}{505}$ or 2.329 V

(e) (2 points)

Solution: $\frac{147}{505}$ or 0.291 A (1 point for value, 1 point for positive sign)

(f) (2 points)

Solution: $\frac{39}{505}$ or 0.077 A (1 point for value, 1 point for positive sign)

(g) (2 points)

Solution: $\frac{453}{2020}$ or 0.224 A (1 point for value, 1 point for positive sign)

(h) (2 points)

Solution: $\frac{609}{2020}$ or 0.301 A (1 point for value, 1 point for positive sign)

(i) Treat the 18Ω resistor as the load for the following subparts.

i. (3 points)

Solution: $\frac{308}{39}$ or 7.897Ω (no partial)

ii. (3 points)

Solution: $\frac{308}{39}$ or 7.897Ω (1 point partial if equal to the previous answer)

iii. (4 points)

Solution: $\frac{72}{13}$ or 5.538 V (partial credit: 2 for identifying that you remove the 18Ω resistor, 1 for any positive voltage less than 9 V)

iv. (4 points)

Solution: $\frac{36}{35}$ or 1.029 A (partial credit: 2 for identifying that you replace the 18Ω resistor with a short, 1 for any positive current)

43. (a) (1 point) _____ **Wheatstone bridge** _____

(b) (2 points)

Solution: a (1), current/voltage difference across the 3Ω resistor is 0 (1)

(c) (1 point) _____ **0 V** _____

(d) (1 point) _____ **$12/7$ or 1.714 V** _____

(e) (2 points) _____ **$14/3$ or 4.67 V** _____

(f) (2 points) _____ **$48/7$ or 6.857 V** _____

(g) (2 points)

Solution: $+2/3$ or $+0.667$ A (1 point for sign, 1 point for value)

(h) (2 points)

Solution: $+1/3$ or $+0.333$ A (1 point for sign, 1 point for value)

(i) (2 points)

Solution: $+12/7$ or $+1.714$ A (1 point for sign, 1 point for value)

(j) (2 points)

Solution: $-6/7$ or -0.857 A (1 point for sign, 1 point for value)

(k) (2 points)

Solution: $24/7$ or 3.429 A (1 point for sign, 1 point for value)

44. (TB #2)

(a) (2 points)


Solution: 25Ω (1 partial if given value is smaller than 50)

(b) (2 points)

Solution: 25Ω (1 partial if equal to value for previous part)

(c) (8 points)


Solution:

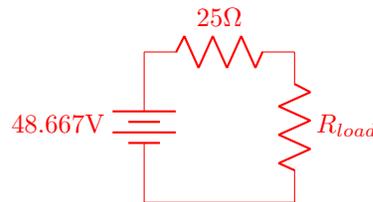

(should look like this with this voltage (48.667 V) and the resistance from the previous problem https://www.allaboutcircuits.com/uploads/thumbnails/Figure_2._Thevenin_equivalent_ (1 for having voltage source/battery, 1 for having resistor, 1 for them being in series, 2 for correct value of equivalent resistor, 3 for correct voltage: +1 partial if voltage is positive and an attempt was made, +1 partial if they show the load resistor was removed, +1 partial if there was either a 3 equation system of KVLs for supermesh or a 6 equation system of KCLs for supernode. NOTE: if the resistance of their resistor is equal to their answer for part (a), give both points for the equivalent resistor).

If they do not close the circuit and/or are missing the load resistor, still give full credit

(d) (8 points)

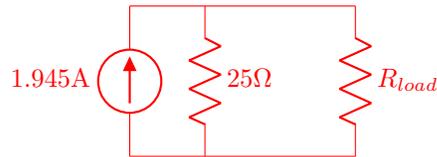Solution:

(should look like this with this current (146/75 or 1.945 A) and the resistance from the first part https://www.allaboutcircuits.com/uploads/thumbnails/Figure_2._Norton_equivalent_ci

(1 for having current source, 1 for having resistor, 2 for them being in parallel, 2 for correct value of equivalent resistor, 5 for correct current: +1 partial if an attempt was made, +1 partial if they show the load resistor was replaced with a short, +1 partial if there was either a 4 equation system of KVLs for supermesh or a 6 equation system of KCLs for supernode. NOTE: if the resistance of their resistor is equal to their answer for part (b), give both points for the equivalent resistor)

If they do not close the circuit and/or are missing the load resistor, still give full credit

45. (a) (1 point)

Solution: $R_1 + R_2$ or anything equivalent

(b) (1 point)

Solution: $\frac{R_c(R_a + R_b)}{R_a + R_b + R_c}$ or anything equivalent

(c) (4 points)

Solution: $R_c = \frac{(R_a + R_b)(R_1 + R_2)}{R_a + R_b - R_1 - R_2}$ (4) (partial credit (only if final answer is wrong): 1 point for multiplying $R_1 + R_2$ by $(R_a + R_b + R_c)$, 1 point for an attempt to simplify this expression (correct result is $R_c(R_a + R_b) = (R_a R_1 + R_b R_1 + R_a R_2 + R_b R_2) + R_c(R_1 + R_2)$, but anything close can earn the point). Give at most 2 points for an +answer which has R_c terms on both sides)

46. (a) (2 points) 20 ms (1 for value, 1 for unit - any equivalent unit/value pair is fine too)
(b) (2 points) 6 mA or .006 A
(c) (2 points) 37% of the original current
(d) (3 points) 76 μ C
(e) (2 points) 0 A

47. (a) (2 points)

Solution: $Q = CV$, so $Q_{C1} = 10\mu\text{F} \cdot 5\text{V} = 50\mu\text{C}$ (1pt). $Q_{C2} = Q_{C3} = 0$ (1pt).

- (b) (3 points)

Solution: $V_a = \frac{50\mu\text{C}}{C_1 + (C_2 || C_3)} = \frac{50\mu\text{C}}{12.4\mu\text{F}} = 4.03\text{V}$

- (c) (4 points)

Solution: $Q_{C1} = C_1 \cdot V_a = 40.3\mu\text{C}$ (2pts), $Q_{C2} = Q_{C3} = (C_2 || C_3) \cdot V_a = 9.7\mu\text{C}$ (2pts)

- (d) (2 points)

Solution: $V_b = Q_{C3}/C_3 = 9.7\mu\text{C}/6\mu\text{F} = 1.62\text{V}$

(e) (5 points)

Solution: No (1pt), both C_2 and C_3 gain a charge for every charge that moves from C_1 , since C_2 and C_3 are in series, so charge appears to increase (2pts). These charges come from a charge separation on the plates between C_2 and C_3 , where positive charges accumulate on one plate and negative charges on the other. (2pts). Also acceptable: Yes (1pt), because the net charge here is always zero and only redistributed (2pt). When the switch is closed, positive charges move from C_1 to C_2 , causing negative charge to build up on the other plate, causing positive charge to build up on C_3 , causing negative charge to build up on the other plate, moving positive charges back to C_1 . (2pt)

48. (a) (4 points)

Solution: $B = \mu_0 n I = \mu_0 (500/0.01)(3) = 0.188\text{T}$

(b) (2 points)

Solution: from right-hand rule: curl fingers counter-clockwise, thumb points out of the page

(c) (2 points)

Solution: it does not experience a force, the magnetic field is constant and the charge is stationary.

(d) (2 points)

Solution: 0, it does not experience a force

(e) (4 points)

Solution: $\frac{\Delta B}{\Delta t} = \mu_0 n \frac{\Delta I}{\Delta t} = \mu_0 (500/0.01)(2) = 0.126 \text{T/s}$

(f) (2 points)

Solution: feels a force down - the increasing magnetic field out of the page creates a clockwise electric field

(g) (4 points)

Solution: $3.15 \times 10^{-3} \text{N}$: $E = -\frac{r}{2} \cdot \frac{\Delta B}{\Delta t}$, $F = QE = (0.5)(.1/2)(0.126) = 3.15 \text{mN}$

Hands-On Tasks

49. (a) (4 points)

Solution: 4 points for building any working circuit on the breadboard

(b) (4 points)

Solution: answers may vary, but a typical answer may be a voltage divider with a known and unknown resistor in series. 4 points for a valid schematic with at least 3 components, -0.5pt per unlabeled component

(c) (6 points)

Solution: 3 pts for reasonable justification for component values, 3 pts for discussion on configuration

(d) (4 points)

Solution: measurements should only be voltages in the circuit, -1pt for incorrect sig-figs

(e) (4 points)

Solution: 3 pts for correct value from voltage measurements and known resistances, 1 pt for correct sig figs in the mystery resistor. note that known resistances are to the specified tolerance

(f) (4 points)

Solution: 2 pts for correct measurement (56 ohm), 2 pts for correct error

(g) (6 points)

Solution: 3 pts for reasonable sources of errors, 3 pts for reasonable improvements

50. (a) (1 point) _____ **50 mA** _____
(b) (3 points)

Solution: 2.6V (1pt), forward current of 20mA (1pt) and ambient temperature of 25°C (1pt)

- (c) (2 points)

Solution: no (.5pt), this would put 3V across the LED and cause a high current to flow (1pt), which can shorten the lifespan or even burn out the LED (.5pt).

- (d) (2 points)

Solution: schematic should have a battery (.5pt), resistor (.5pt) in series (.5pt) with the LED (.5pt)

- (e) (2 points)

Solution: current-limiting resistor (1pt) is in series (1pt) with the LED, since the LED voltage is fixed, the resistor takes the rest of the voltage drop.

(f) (1 point)

Solution: $\frac{3V-2.1V}{20mA} = 45\Omega$

(g) (1 point)

Solution: 47 Ω resistor

(h) (4 points)

Solution: 4 points for building it

(i) (4 points)

Solution: $\frac{3.2V-2.1V}{47\Omega} = 23mA$ (2pt), $\frac{2.9V-2.6V}{47\Omega} = 6.4mA$ (2pt)

(j) (2 points) _____ $\approx 37.5mA$ _____

(k) (2 points)

Solution: no, max current @ 70C is 30mA

(l) (2 points)

Solution: $\frac{3V-2.1V}{37.5mA} = 24\Omega$ (1pt), 22Ω (1pt)

(m) (4 points)

Solution: 4 pts for correctly measuring the current.

(n) (4 points)

Solution: 4 pts for reasonable answer

51. (a) (5 points)

Solution: Schematic should have a battery or some kind of labeled input voltage (1pt), two resistors in series as a divider (1pt), a labeled output between those (1pt), and a labeled (1pt) load resistor connected in parallel to one of those resistors (1pt).

(b) (5 points)

Solution: answers may vary, should be something like $V_{out} = V_{in} \cdot \frac{R_2 || R_L}{R_1 + (R_2 || R_L)}$ where $R_2 || R_L = \frac{R_2 R_L}{R_2 + R_L}$. 2 pts for a correct voltage divider formula, 3 pts for correctly including the load resistor.

(c) (4 points)

Solution: 2 pts for resistors in a ratio of 5:7, 2 pts for 22Ω and 15.7Ω or less.

(d) (6 points)

Solution: answers may vary, the best way would be a 22Ω with a 22Ω in parallel with a 56Ω . 1pt for labeling input/output, 5 pts for the ideal circuit. Give 4 pts for an attempt at approximating ideal values, 2 pts for any voltage divider using the given resistors, and 0 pts for including resistors that were not provided.

(e) (4 points)

Solution: 4 points for building the circuit they drew

(f) (4 points)

Solution: 2 pts for a measured input voltage, 2 pts for a measured output voltage, -1pt for incorrect sig-figs

(g) (2 points)

Solution: 2 pts for a correctly measured output voltage

(h) (4 points)

Solution: 4 points for voltages across each resistor, -1pt for each missing/incorrect measurement

(i) (5 points)

Solution: 5 points for correct calculations, -1pt for incorrect sig-figs

(j) (6 points)

Solution: 2 pts for discussing whether or not the design meets the spec, 4 pts for discussing at least two sources of error e.g. resistor tolerance, input voltage variation